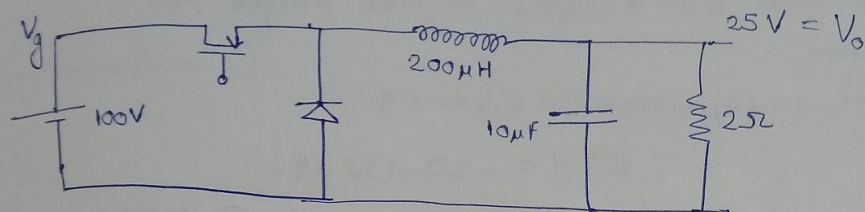


Buck converter design with voltage control and active emi filter

Buck Converter



$f_s \rightarrow$ switching frequency 250 kHz PWM.

I) Design of closed loop control.

$D = 0.25$ (Duty Cycle)

Small signal Model.


$$\hat{V}_o = G_{vd} \hat{d} + G_{vg} \hat{V}_g - Z_{out} \hat{i}_{out}(s)$$

Output Voltage

$$G_{vd} = \frac{V_g}{(LC) \left[s^2 + \frac{s}{rC} + \frac{1}{LC} \right]}$$


$$Z_{out}(s) = \frac{s}{C \left[s^2 + \frac{s}{rC} + \frac{1}{LC} \right]}$$
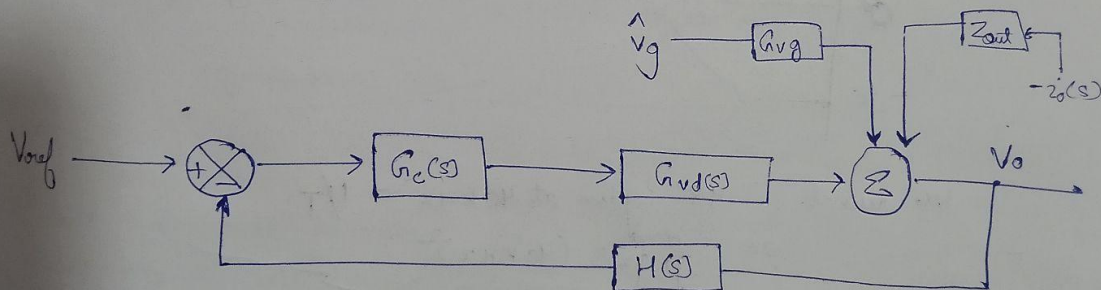
$$G_{vg} = \frac{D}{(LC) \left[s^2 + \frac{s}{rC} + \frac{1}{LC} \right]}$$




$H(s) \rightarrow$ sensor gain

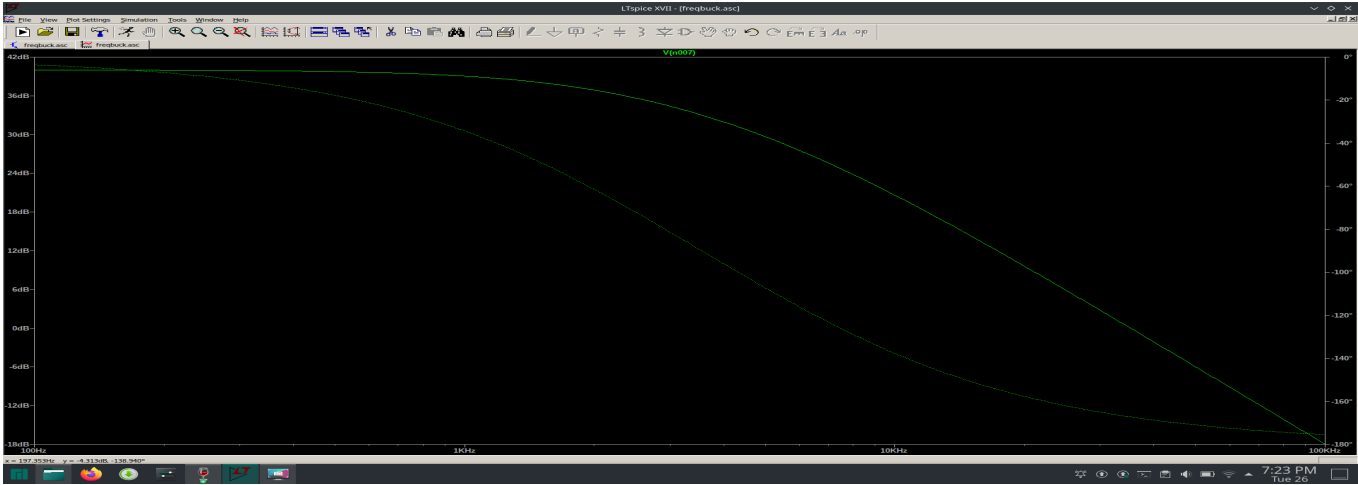
$G_c(s) \rightarrow$ compensator to be designed.



Gvd

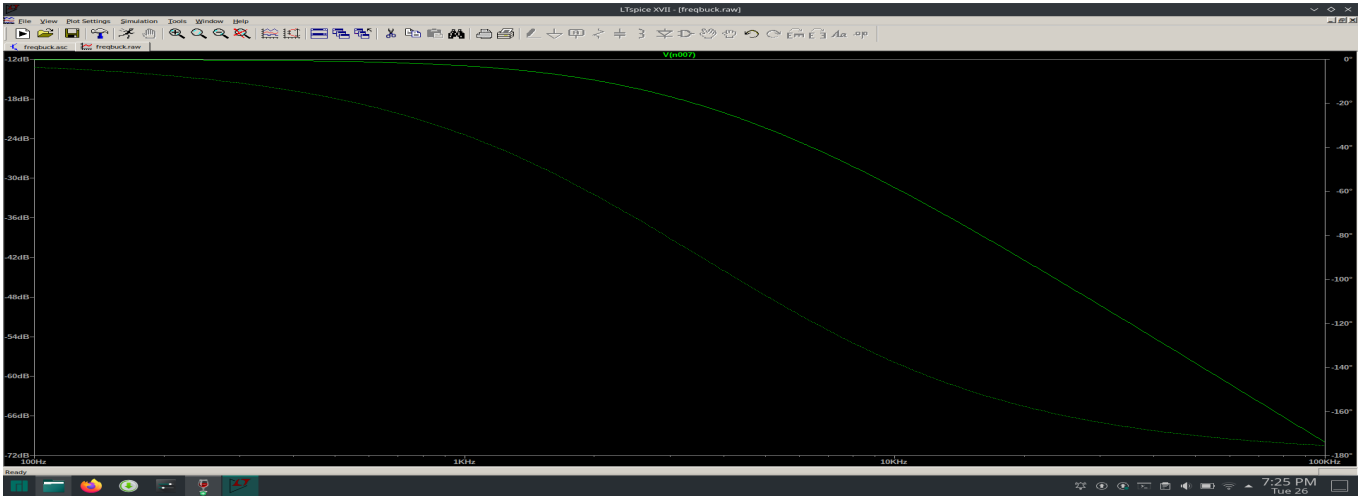

Gvg

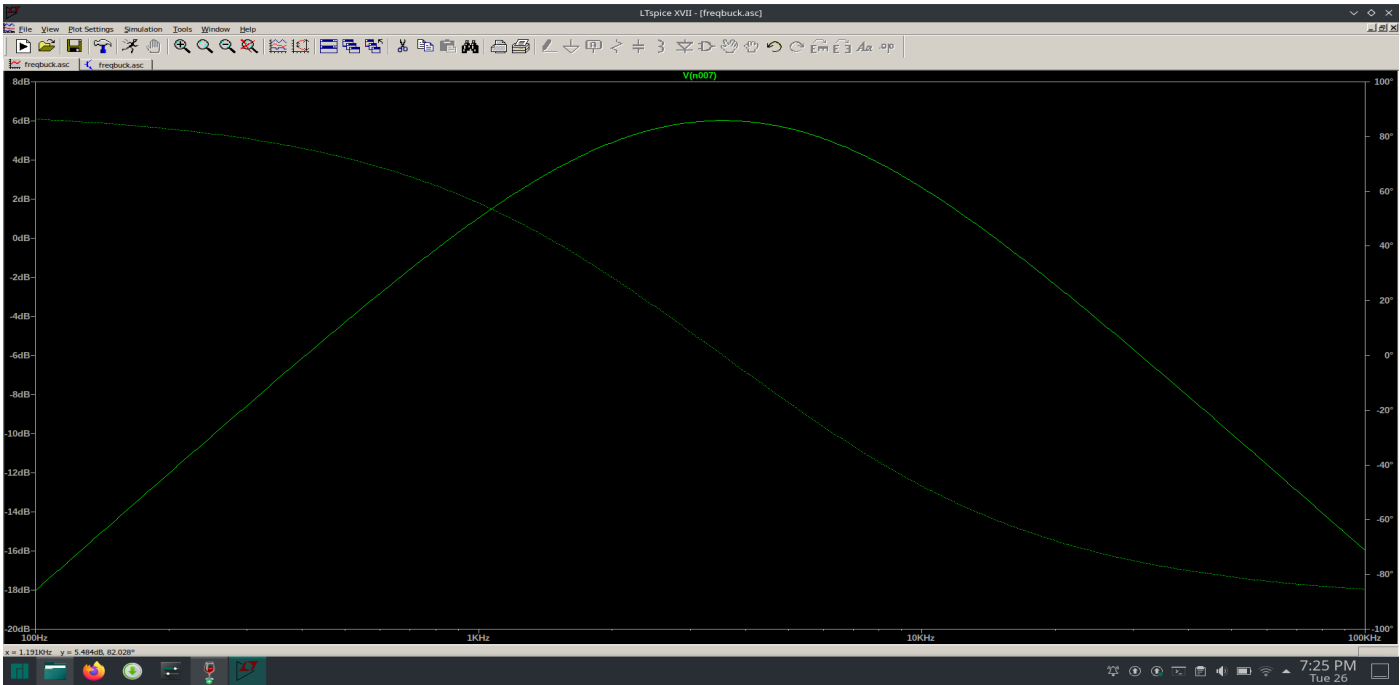

Zout

Let's design $G_c(s)$

say we want $BW \rightarrow 40 \text{ kHz}$ & Phase Margin $\sim 60^\circ$
then


for uncompensated $T = G_{vd}(s) \times H(s)$

$$\|T\| = -22.133 \text{ dB}$$

$$\angle T(s) = -168.66^\circ @ 40 \text{ kHz}$$

For zero steady state error
we introduce a pole at $s=0$.
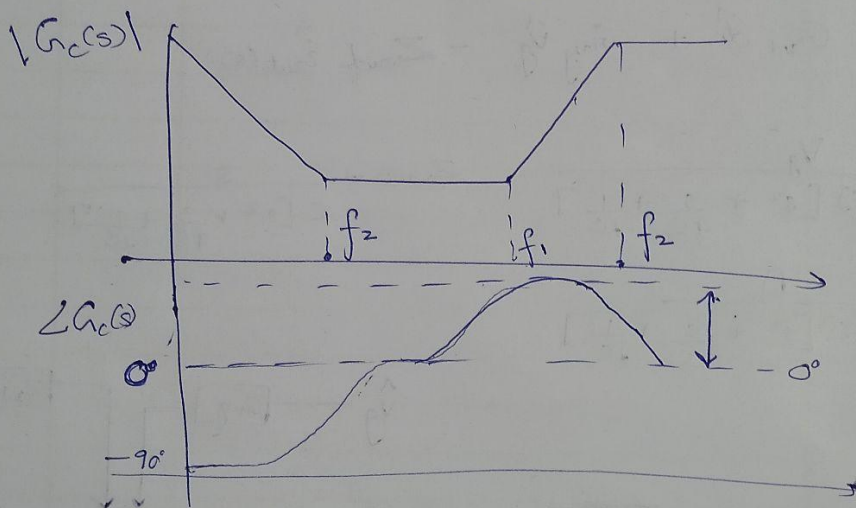
$$\text{Let } G_c(s) = k \left[1 + \frac{\omega_z}{s} \right] \left[\frac{s + \omega_1}{s + \omega_2} \right]$$



We want 48° gain at $40 \text{ kHz} = 1/T$

$$\text{so } f_1 f_2 = (40 \text{ kHz})^2$$

$$\& \text{ let } a = \frac{1 + \sin(48^\circ)}{1 - \sin(48^\circ)} \approx 6.8$$

then

$$f_1 = \frac{1}{\sqrt{a} T} \quad f_2 = \frac{\sqrt{a}}{T}$$

$$\omega = 2\pi f$$


$$\Rightarrow f_1 = 15354 \text{ Hz}$$

$$f_2 = 104203 \text{ Hz}$$

select $f_z \ll 40\text{kHz}$ to avoid phase lag by f_z

here so we choose $f_z = 2\text{kHz}$

Implementation.

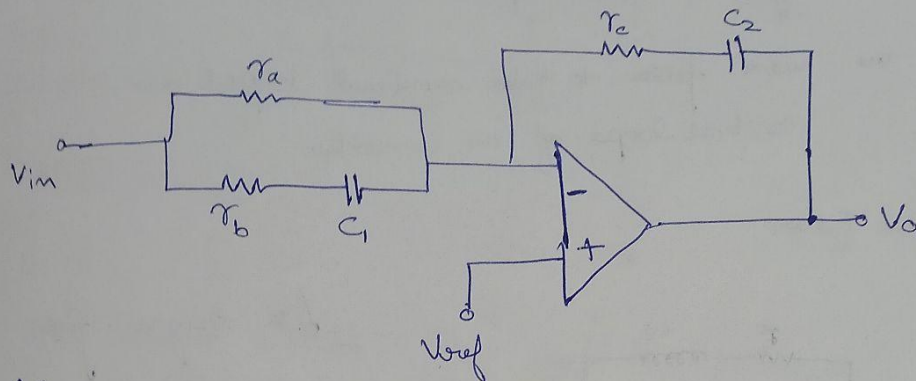

For AC

$$\frac{V_o}{V_{in}} = \frac{\left(r_c + \frac{1}{sC_2}\right)}{r_a \parallel \left(r_b + \frac{1}{sC_1}\right)}$$

$$\Rightarrow \cancel{r_c} = \left(\frac{r_c}{r_a \parallel r_b}\right) \left[1 + \frac{1}{sC_2 r_c}\right] \left[\frac{s + 1/[r_a + r_b C_1]}{s + 1/[r_b C_1]}\right]$$


Plugging in values for required $G_c(s)$ we get
(without adjusting gain yet)

$$r_c = 6.1\text{k}\Omega \quad C_1 = 1.45\text{mF} \quad C_2 = 13\text{mF}$$


$$r_a = 6.55\text{k}\Omega \quad r_b = 1\text{k}\Omega$$

At last we add another gain stage. (also since it was inverting, so we need another inverting stage)

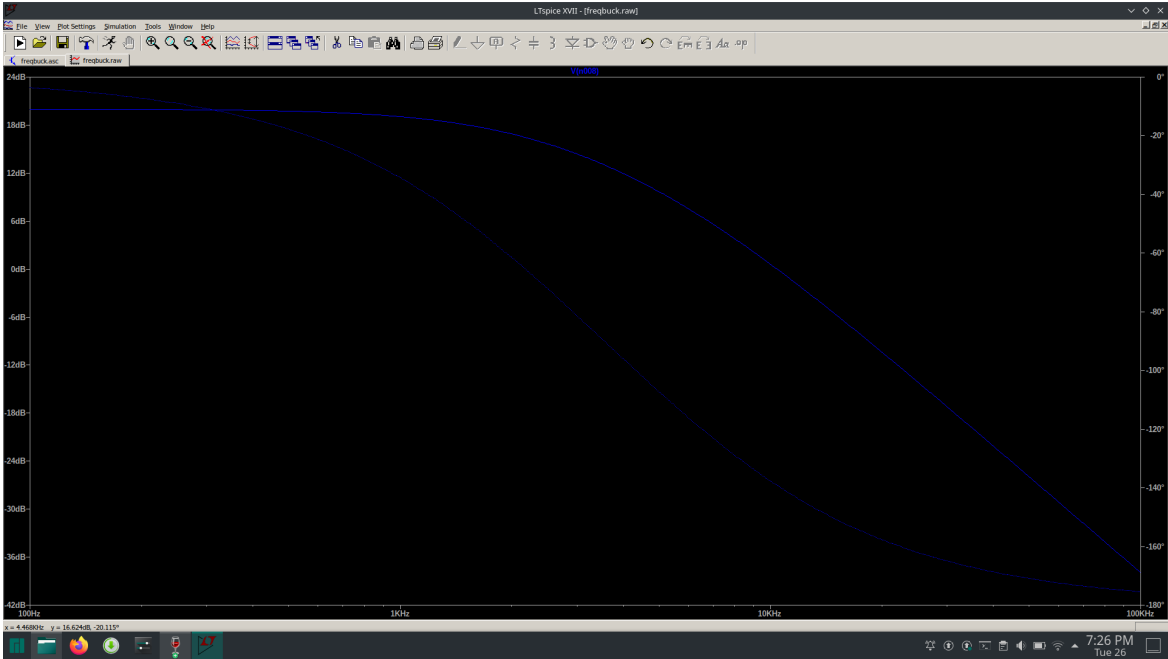* The need to use 2 stages arises due to finite GBW product of opamps.



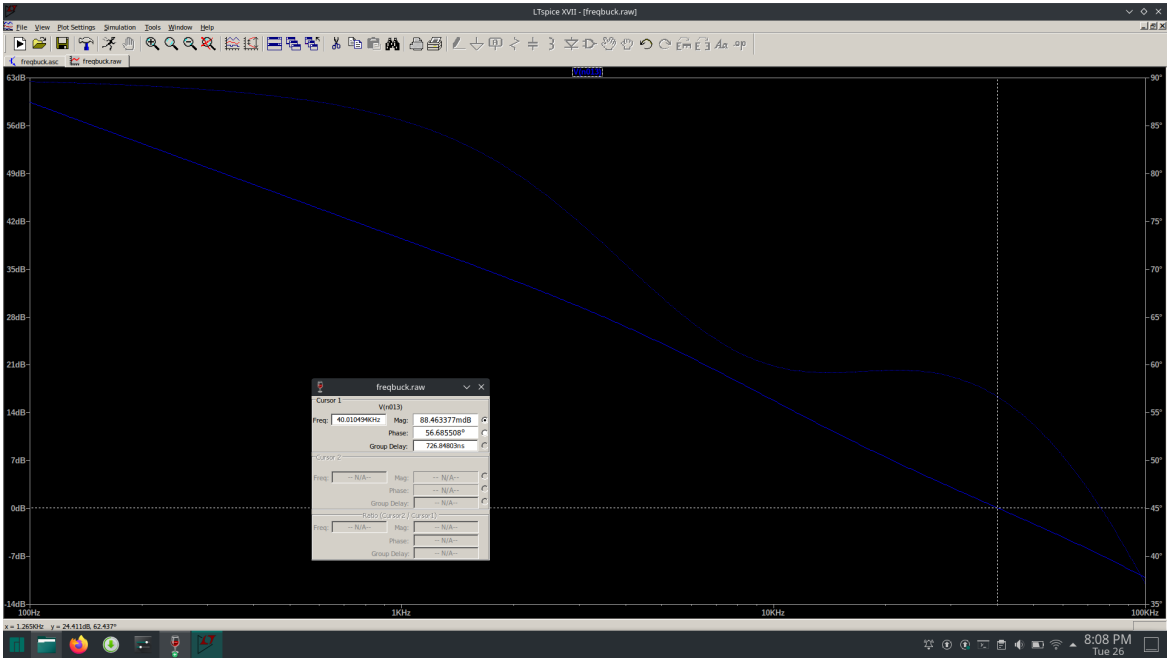Open Loop Transfer Function Uncompensated



Compensated open loop transfer function


we get our G_c as required.

Now to design EMI Filter.

To design an active & passive EMI Filter.

we want filter to have minimal impact on control loops of the converter.

① Passive Filter.

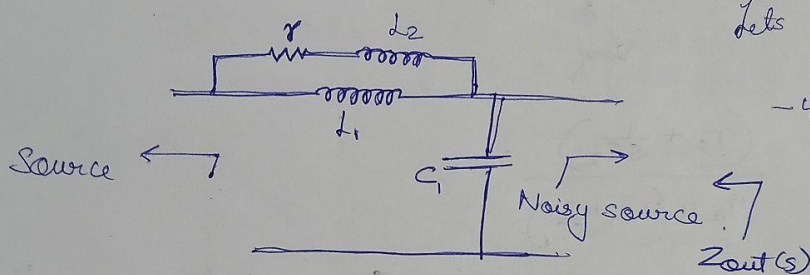

Let's design for

-40 dB at
250 kHz

$$\text{Also } Z_{out}(s) \ll \frac{R}{D^2}$$

(The detailed design is skipped here, its based on Ch-17 of Fundamentals of Power Electronics by Erickson).


$$L_1 = 5.5 \mu\text{H} \quad L_2 = 2.55 \mu\text{H} \quad C = 22 \mu\text{F}$$

$$r = 0.5 \Omega$$



Design of active EMI Filter

Modelling

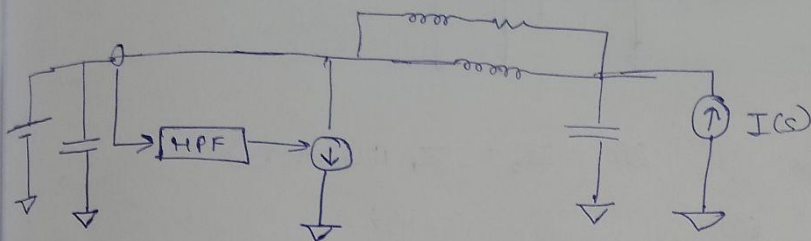The Buck Converter side can be modelled as a current source



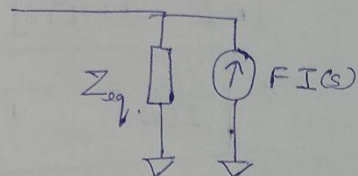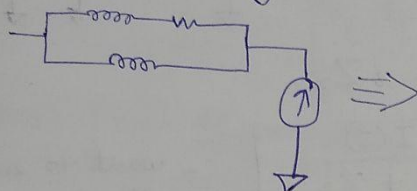
The current is sensed, then high pass filtered & ~~passed through~~ shunted to ground.




Norton Equivalent

At high freq. the input voltage source can be seen as zero impedance however parasitic inductances (we are concerned with 100 kHz > frequencies) are present.

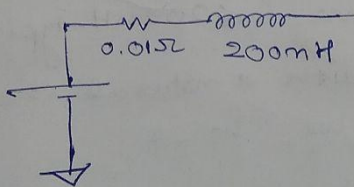so typical ~~values~~ of source at high freq.




at high. freq

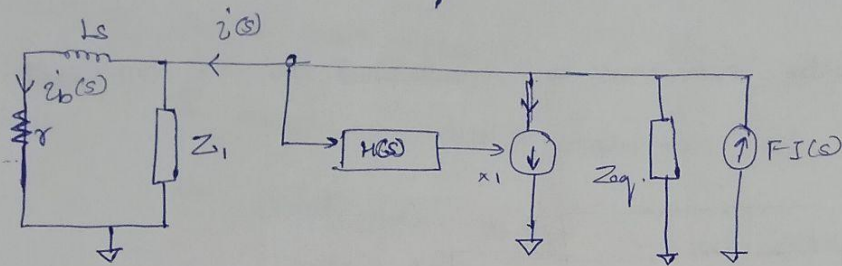

$$i_b(s) = \frac{i(s) Z_1}{Ls + r}$$
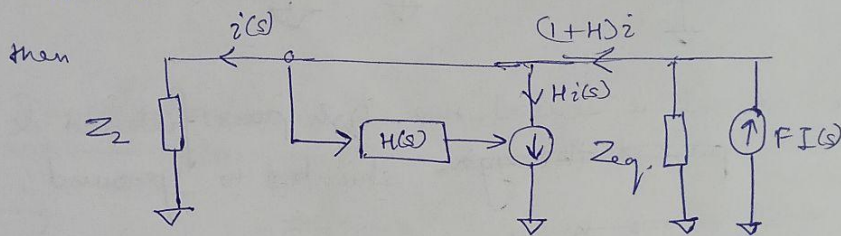
$$\text{let } Z_2 = Z_1 \parallel (Ls + r)$$



$$[FI - (1+H)i] Z_{eq} = i Z_2$$


$$\Rightarrow \frac{i(s)}{I(s)} = \frac{F(s) I(s)}{1 + H + \left(\frac{Z_2}{Z_{eq}} \right)}$$


want to minimise this term.

$\frac{Z_2}{Z_{eq}}$ is a problematic term & can lead to stability problems so we want to minimise it. so that $\frac{Z_2}{Z_{eq}} \ll 1$ for lower freq.


& design of $H(s)$ becomes easier.

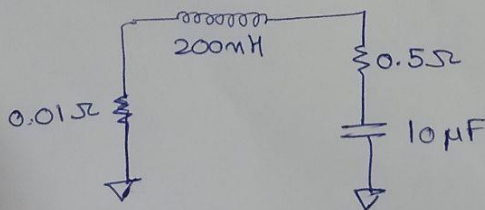the parasitic inductance ($\leq 200\text{mH}$ typical) can cause resonance with a natural choice of Z_1 as capacitor so we choose.



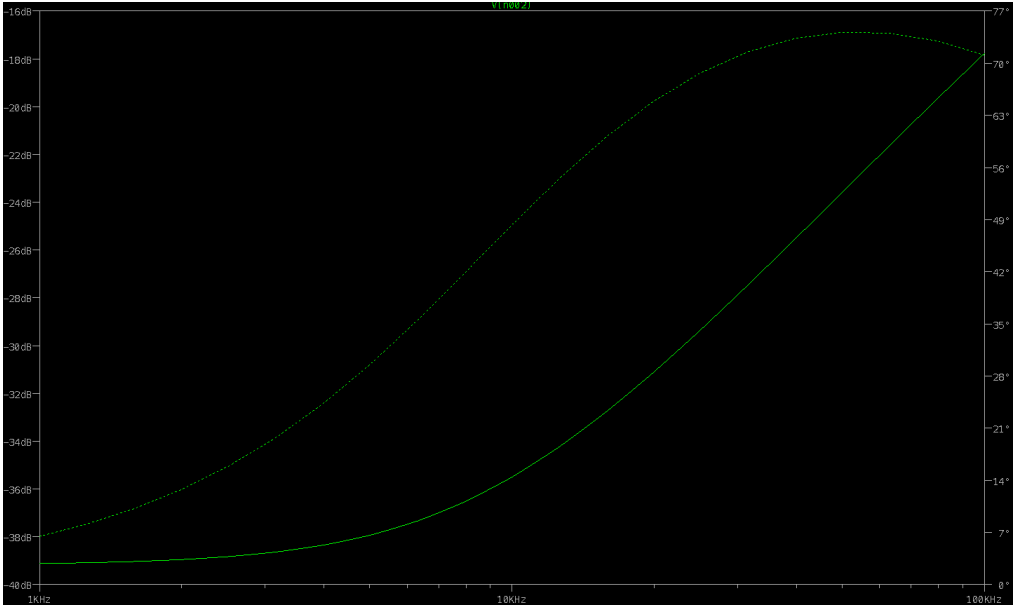


Z_2

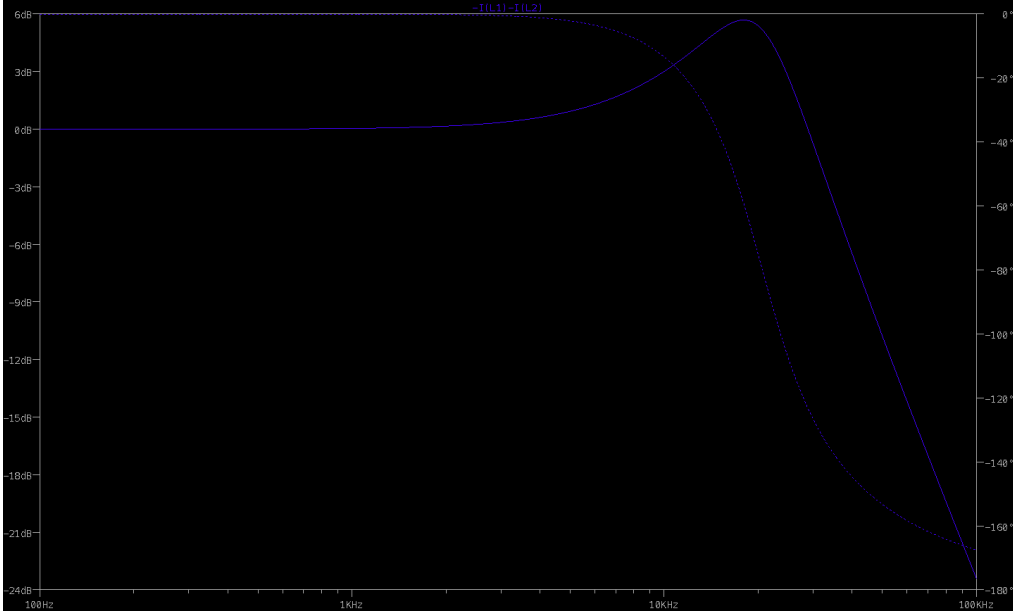

$F(s)$

$I(s)$ has ~~se~~ components at switching frequencies & its multiples only. so a slight dip therefore isn't a problem in $F(s)$ at lower frequencies...

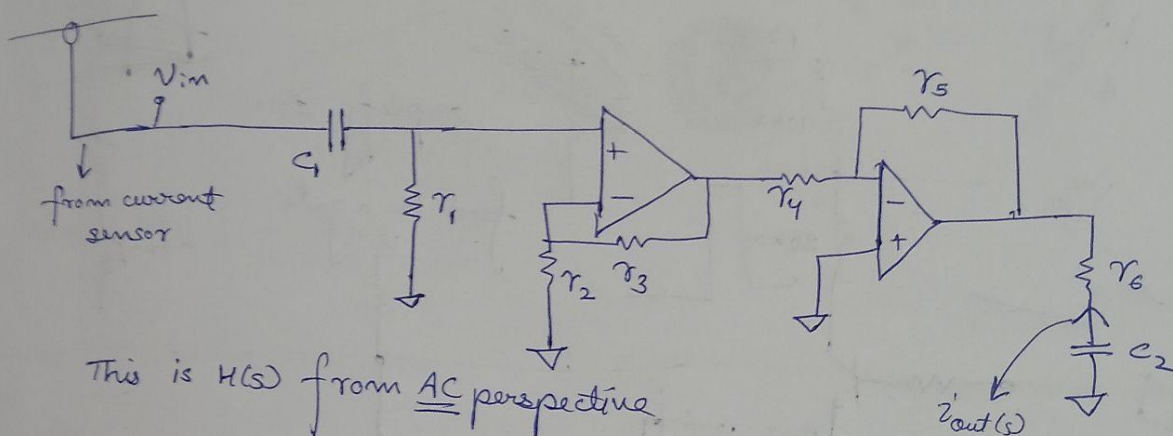let $H(s)$ be 2nd order high Pass filter
(actually its a voltage to current converter)



This is $H(s)$ from AC perspective


$$\frac{i_{out}(s)}{V_{in}(s)} = \frac{1}{r_6} \left(\frac{r_5}{r_4} \right) \left(1 + \frac{r_3}{r_2} \right) \left(\frac{s^2}{(s + 1/r_1 C_1)(s + 1/r_6 C_2)} \right)$$

we can play around with these values
but must ensure stability & sufficient gain
to suppress EMI.

In this example. $C_1 = 10\text{mF}$ $r_1 = 50\text{k}\Omega$ $r_3 = 6\text{k}\Omega$
 $r_2 = 1\text{k}\Omega$


$r_5 = 7\text{k}\Omega$ $r_4 = 1\text{k}\Omega$

$C_2 = 2\mu\text{F}$ $r_6 = 1\Omega$

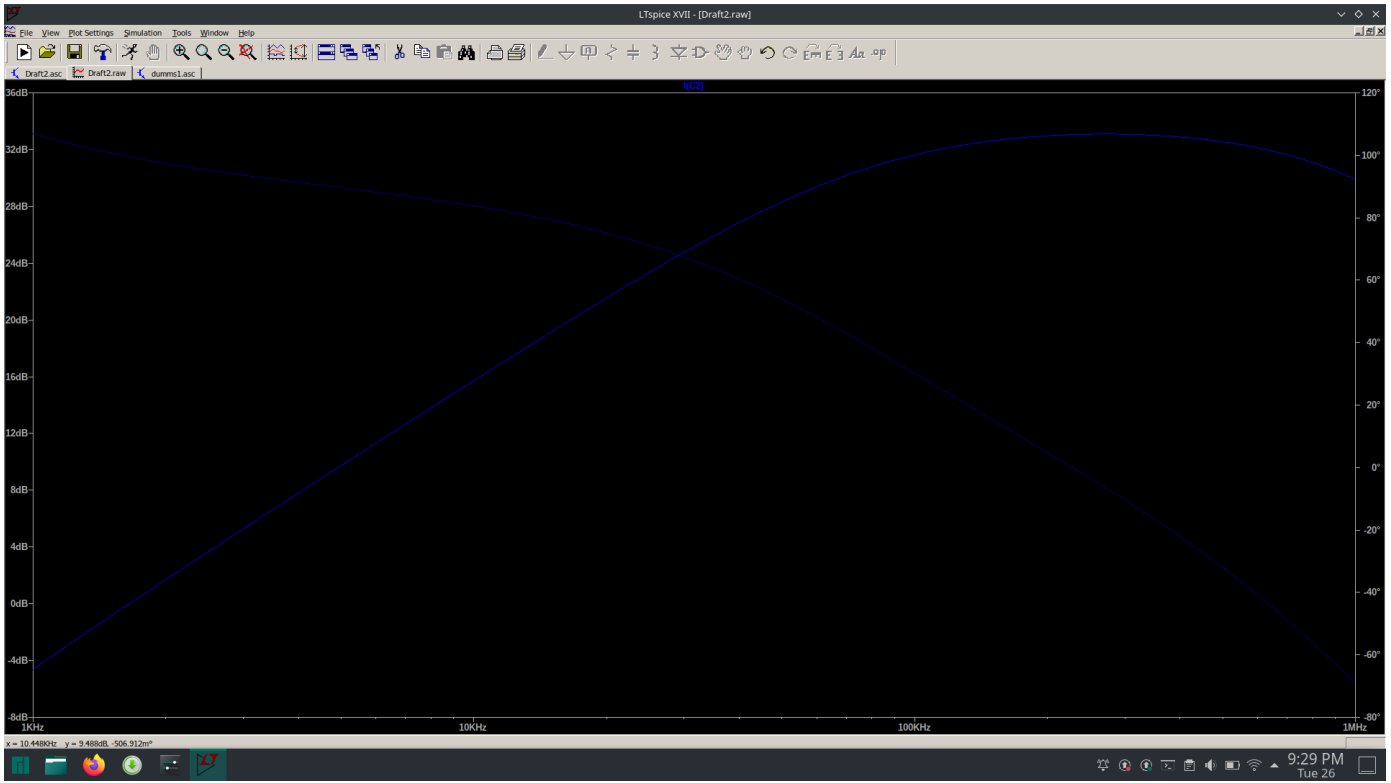


The high pass filter, the above plot is for output current vs input voltage $i_{out}(s)/v_{in}(s)$


The complete circuit

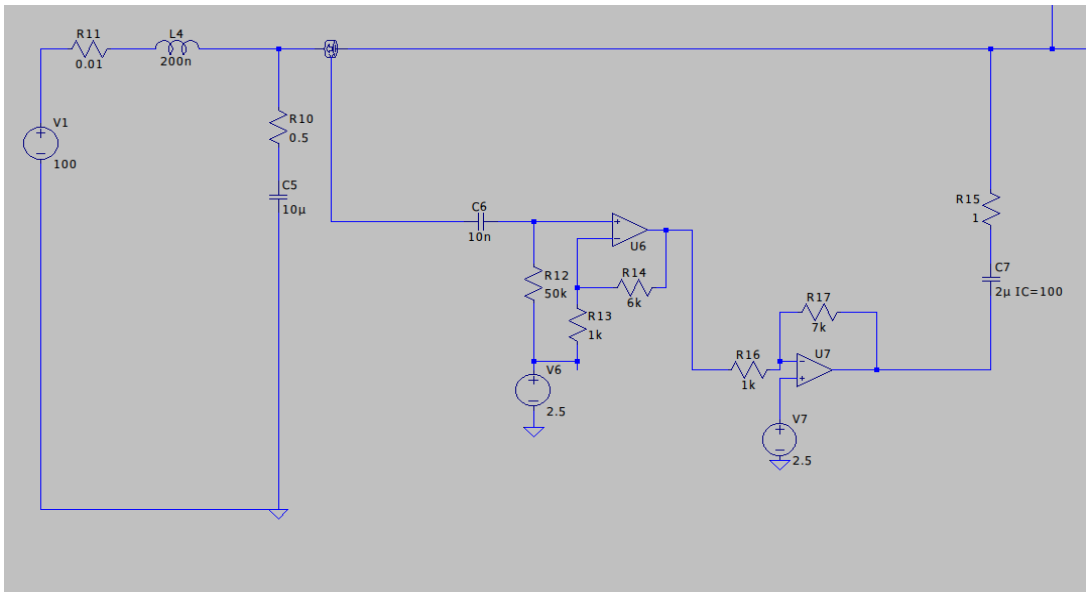

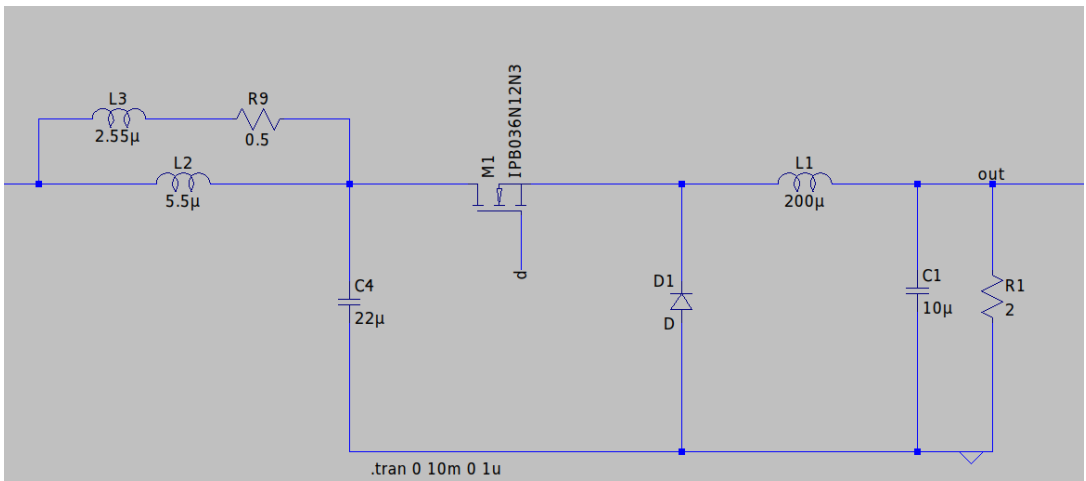
The input voltage source and Z2 and active EMI filter




Passive EMI filter and Buck converter

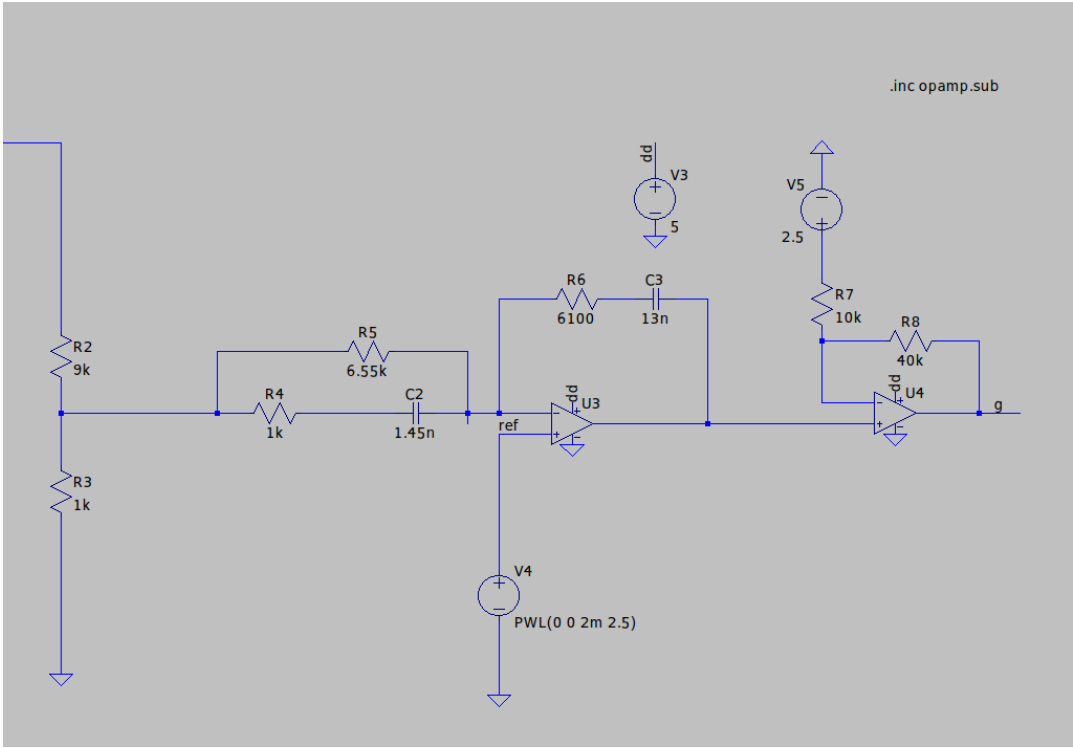


The closed loop controller

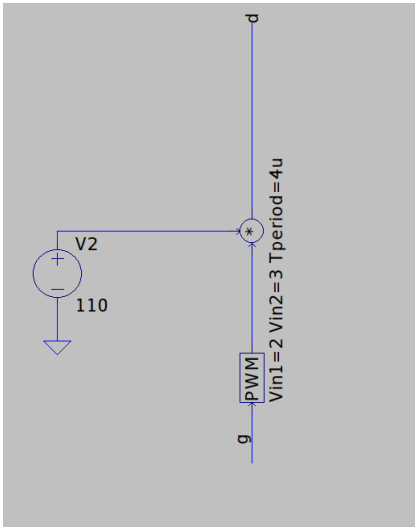

PWM block form the library

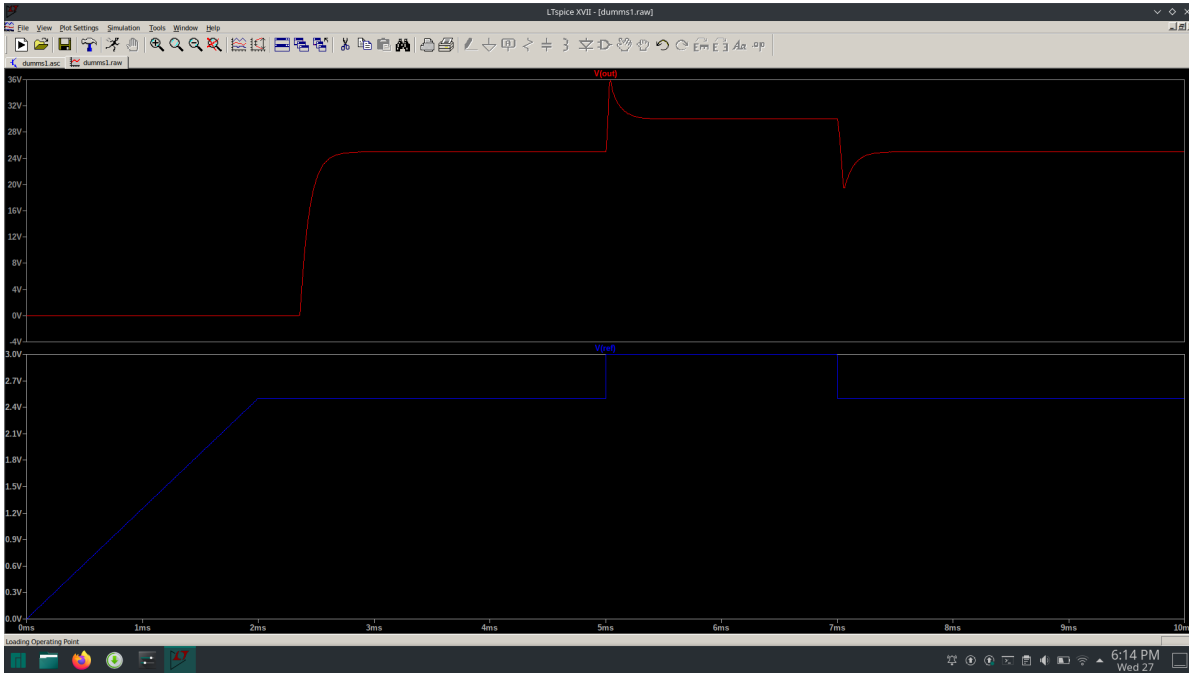

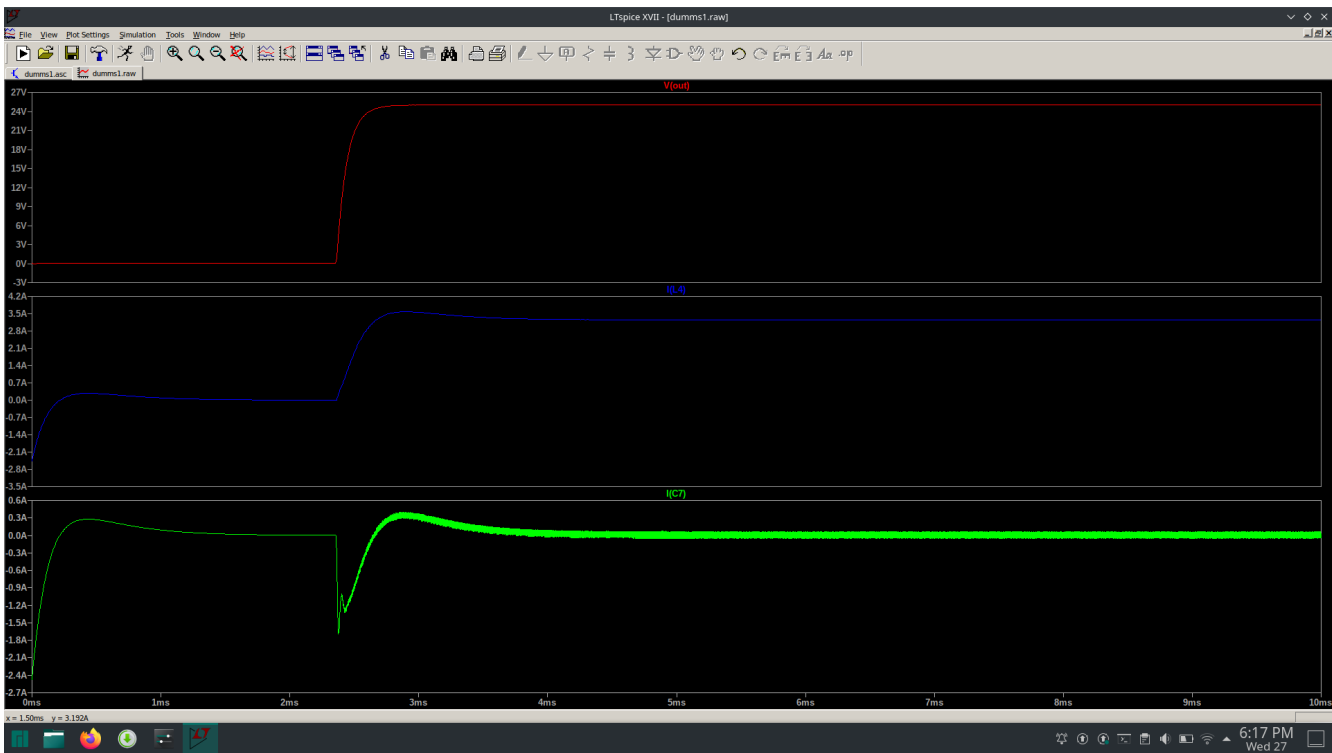Output Voltage vs reference (soft start to avoid initial overvoltage at input)



The currents, Blue waveform -> Battery current (very clean)!, Green waveform -> the current though the active EMI filter, the high frequency components are shunted by active EMI filter, red curve is output voltage